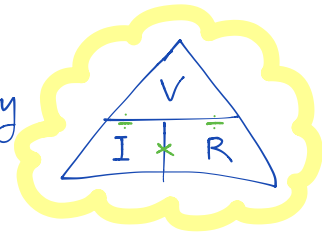


## Ohm's Law Practice

Name: Key  
Date:  
Block:

1. An alarm clock draws **0.500 A** of current when connected to a **120.0 volt** circuit. Calculate its resistance.

$$V = 120.0 \text{ V}$$

$$I = 0.500 \text{ A}$$

$$R = ?$$

$$R = \frac{V}{I}$$

$$R = \frac{120.0 \text{ V}}{0.500 \text{ A}} = \boxed{240 \Omega}$$

2. A subwoofer needs a household voltage of **110.0 V** to push a current of **5.5 A** through its coil. What is the resistance of the subwoofer?

$$V = 110.0 \text{ V}$$

$$I = 5.5 \text{ A}$$

$$R = ?$$

$$R = \frac{110.0 \text{ V}}{5.5 \text{ A}} = \boxed{20 \Omega}$$

3. A walkman uses a standard **1.5 V** battery. How much resistance is in the circuit if it uses a current of **0.01 A**?

$$V = 1.5 \text{ V}$$

$$I = 0.01 \text{ A}$$

$$R = ?$$

$$R = \frac{V}{I}$$

$$= \frac{1.5 \text{ V}}{0.01 \text{ A}} = \boxed{150 \Omega}$$

4. A circuit contains a **1.5 volt** battery and a bulb with a resistance of **3.0 ohms**. Calculate the current.

$$V = 1.5 \text{ V}$$

$$I = ?$$

$$R = 3.0 \Omega$$

$$I = \frac{V}{R}$$

$$= \frac{1.5 \text{ V}}{3.0 \Omega} = \boxed{0.5 \text{ A}}$$

5. What current flows through a hair dryer plugged into a **120.0 Volt** circuit if it has a resistance of **25.0 ohms**?

$$V = 120.0 \text{ V}$$

$$I = ?$$

$$R = 25.0 \Omega$$

$$I = \frac{V}{R}$$

$$= \frac{120.0 \text{ V}}{25.0 \Omega} = \boxed{4.8 \text{ A}}$$

6. What happens to the current in a circuit if a 1.50-volt battery is removed and is replaced by a 3.00-volt battery?

$$V = 1.50 \text{ V} \rightarrow 3.0 \text{ V}$$

$$I = 1.5 \text{ A} \rightarrow 3.0 \text{ A}$$

$$R = \text{assume } R \text{ is constant} = 1 \Omega$$

if you double the voltage,  
the current also  
doubles!

7. If a toaster produces 12.0 ohms of resistance in a 120.0-volt circuit, what is the amount of current in the circuit?

$$V = 120.0 \text{ V}$$

$$I = ?$$

$$R = 12.0 \Omega$$

$$\begin{aligned} I &= \frac{V}{R} \\ &= \frac{120.0 \text{ V}}{12.0 \Omega} \\ &= 10 \text{ A} \end{aligned}$$

8. A 12.0 Volt car battery pushes charge through the headlight circuit resistance of 10.0 ohms. How much current is passing through the circuit?

$$V = 12.0 \text{ V}$$

$$I = ?$$

$$R = 10.0 \Omega$$

$$\begin{aligned} I &= \frac{V}{R} \\ &= \frac{12.0 \text{ V}}{10.0 \Omega} \\ &= 1.2 \text{ A} \end{aligned}$$

9. How much voltage would be necessary to generate 10.0 amps of current in a circuit that has 5.00 ohms of resistance?

$$V = ?$$

$$I = 10.0 \text{ A}$$

$$R = 5.00 \Omega$$

$$\begin{aligned} V &= I \times R \\ &= (10.0 \text{ A})(5.00 \Omega) \\ &= 50.0 \text{ V} \end{aligned}$$

10. An electric heater works by passing a current of 100.0 A through a coiled metal wire, making it red hot. If the resistance of the wire is 1.100 ohms, what voltage must be applied to it?

$$V = ?$$

$$I = 100.0 \text{ A}$$

$$R = 1.100 \Omega$$

$$\begin{aligned} V &= I \times R \\ &= (100.0)(1.100 \Omega) \\ &= 110.0 \text{ V} \end{aligned}$$

11. A light bulb has a resistance of 5.0 ohms and a maximum current of 10.0 A. How much voltage can be applied before the bulb will break?

V = ?

$$V = I \times R$$

$$= (10.0 \text{ A})(5.0 \Omega)$$

$$= 50 \text{ V}$$

I = 10.0 A

R = 5.0 Ω

12. What happens to the current in a circuit if a 10.0 Ω resistor is removed and replaced by a 20.0 Ω resistor?

V = assume voltage stays constant

V = 1

$$I = \frac{V}{R}$$

$$I = \frac{1}{20}$$

I = ?



$$= \frac{1}{10} = 0.1 \text{ A}$$

$$= 0.05 \text{ A}$$

R = 10.0 Ω → 20.0 Ω

If you double the resistance, current is halved

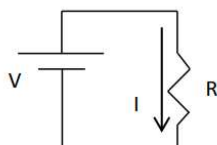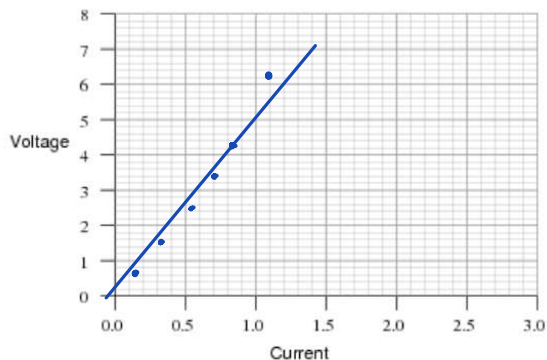13. Suppose you did a lab with this simple circuit and got the following data. Plot the points of the provided graph.



y-axis x-axis

Voltage (V)	Current (A)
0.65	0.12
1.41	0.29
2.55	0.51
3.28	0.67
4.11	0.81
6.15	1.23

\* challenge!

a) What mathematical relationship do you see between voltage and current?

linear relationship


\*

b) Is the resistance constant?


$$\frac{\text{Rise}}{\text{Run}} = \frac{\text{Voltage}}{\text{current}} = \text{Resistance}$$

Yes!

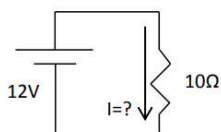
14. Solve for the unknown in each of these circuits.



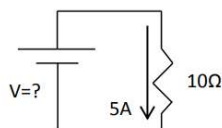
$$I = \frac{12\text{V}}{10\Omega} = 1.2 \text{ A}$$



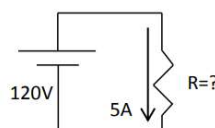
$$V = (5\text{A})(10\Omega) = 50 \text{ V}$$



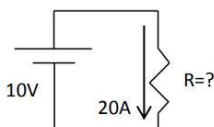
$$R = \frac{120\text{V}}{5\text{A}} = 24 \Omega$$


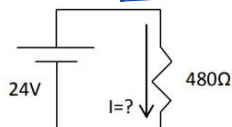
$$R = \frac{10\text{V}}{20\text{A}} = 0.5 \Omega$$


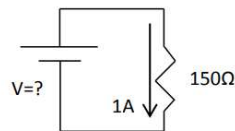
$$I = \frac{24\text{V}}{480\Omega} = 0.05 \text{ A}$$



$$V = (1\text{A})(150\Omega) = 150 \text{ V}$$